

EECS 16B HW02

Bryan Ngo

2020-01-25

1 Fundamental Theorem of Solutions to Differential Equations

1.a

Theorem 1. Given $\phi_1(x) = e^x$ and $\phi_2(x) = \sum_{n=0}^{\infty} \frac{x^n}{n!}$, $\phi_1(x) = \phi_2(x)$.

Proof. Proving the derivative property,

$$\frac{d}{dx} \phi_1(x) = \frac{d}{dx} e^x = e^x = \phi_1(x) \quad (1)$$

$$\frac{d}{dx} \phi_2(x) = \frac{d}{dx} \sum_{n=0}^{\infty} \frac{x^n}{n!} = \sum_{n=0}^{\infty} \frac{n x^{n-1}}{n!} = \sum_{n=1}^{\infty} \frac{x^{n-1}}{(n-1)!} = \phi_2(x) \quad (2)$$

where we are allowed to shift the index because any singular n terms cancel to zero. Proving the initial condition,

$$\phi_1(0) = e^0 = 1 \quad (3)$$

$$\phi_2(0) = \sum_{n=0}^{\infty} \frac{0^n}{n!} = \frac{0^0}{0!} + \cancel{\frac{0^1}{1!}} + \cancel{\frac{0^2}{2!}} + \cancel{\dots} = 1 \quad (4)$$

□

1.b

Theorem 2. Given $\phi_1(x) = \cos(x)$ and $\phi_2(x) = \cos(-x)$, $\phi_1(x) = \phi_2(x)$.

Proof. Proving the derivatives,

$$\frac{d^2}{dx^2} \phi_1(x) = \frac{d^2}{dx^2} \cos(x) = -\cos(x) = -\phi_1(x) \quad (5)$$

$$\frac{d^2}{dx^2} \phi_2(x) = \frac{d^2}{dx^2} \cos(-x) = -\cos(-x) = -\phi_2(x) \quad (6)$$

Proving the initial conditions,

$$\phi_1(x) = \phi_2(x) = \cos(0) = 1 \quad (7)$$


$$\frac{d}{dx} \phi_1(0) = -\sin(0) = 0 \quad (8)$$

$$\frac{d}{dx} \phi_2(0) = \sin(0) = 0 \quad (9)$$

□

2 IC Power Supply

2.a

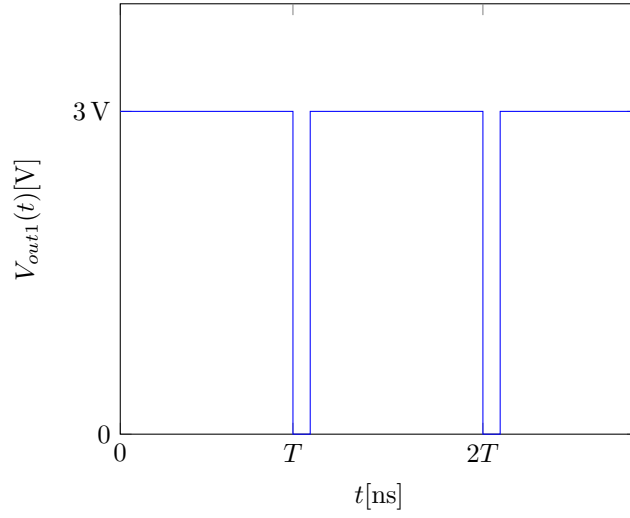



2.b


The generalized expression for V_{DD} can be represented with the differential equation

$$C \frac{d}{dt} V_{DD} + i(t) - \frac{V_s - V_{DD}}{R} = 0 \quad (10)$$

$$\frac{d}{dt} V_{DD} + \frac{V_{DD}}{RC} = \frac{V_s}{RC} - \frac{i(t)}{C} \quad (11)$$

with $i(0) = 0$.

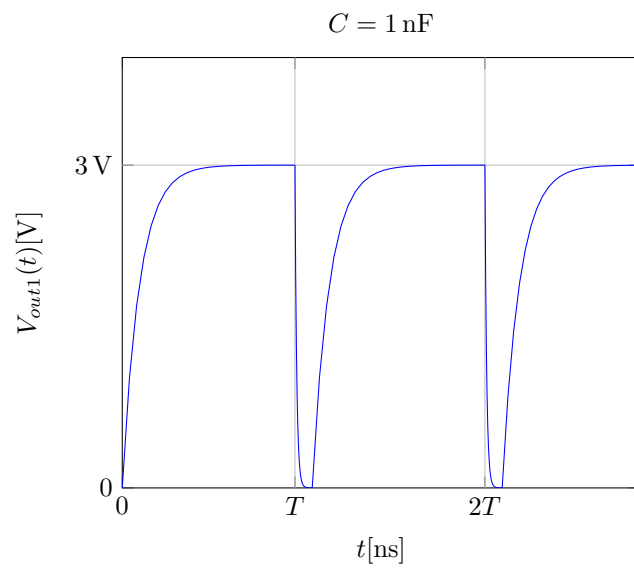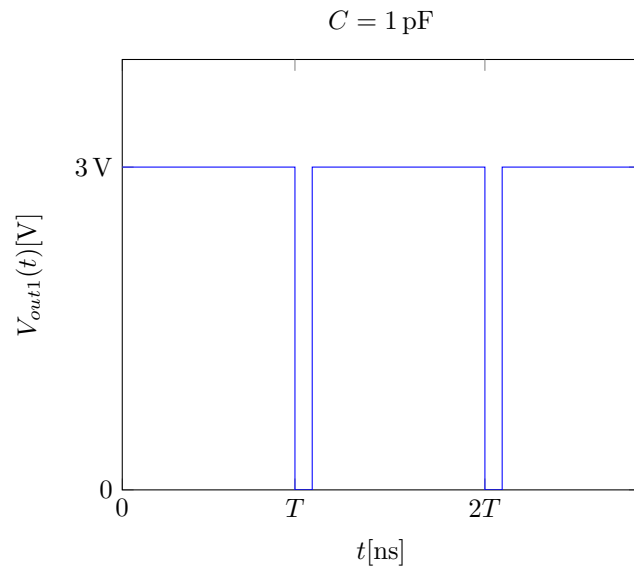

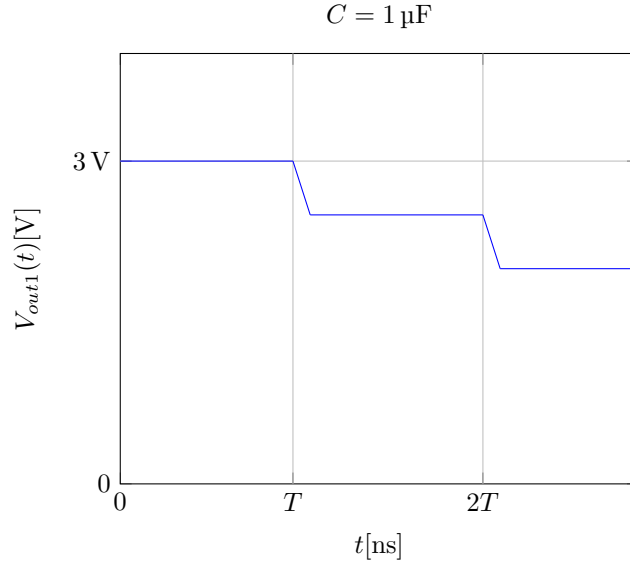

2.c

It is better to have a higher C than a higher R . This is because a higher capacitance means that the capacitor will take longer to discharge completely, resisting larger changes in voltage, possibly outlasting t_p .

3 Simple Scalar DEs Driven by an Input

3.a

Proof. We will prove that $\delta(t) = x_g(t) - y(t) = 0$, thus proving uniqueness. First proving the initial conditions cancel,

$$\delta(t) = x_g(0) - y(0) = x_0 - x_0 = 0 \quad (12)$$

Next, we prove uniqueness of the derivative:

$$\frac{d}{dt} \delta(t) = \frac{d}{dt} (x_g - y) \quad (13)$$

$$= \lambda x_g + \cancel{u(t)} - \lambda y - \cancel{u(t)} \quad (14)$$

$$= \lambda(x_g - y) \quad (15)$$

□

3.b

Proof.

$$x_c(t) = x_0 e^{\lambda t} + \int_0^t u(\tau) e^{\lambda(t-\tau)} d\tau \quad (16)$$

$$x_c(0) = x_0 e^{\lambda \cdot 0} + \int_0^0 u(\tau) e^{\lambda(t-\tau)} d\tau = x_0 \quad (17)$$

$$\frac{d}{dt} x_c(t) = \lambda x_0 e^{\lambda t} + \underbrace{\int_0^t \frac{\partial}{\partial t} u(\tau) e^{\lambda(t-\tau)} d\tau}_{\text{Leibniz integral rule}} + \underbrace{u(t) e^{\lambda(t-t)}}_{\text{FTC}} \quad (18)$$

$$= \lambda x_c(t) + \lambda \int_0^t u(\tau) e^{\lambda(t-\tau)} d\tau + u(t) \quad (19)$$

$$= \lambda x_c(t) + u(t) \quad (20)$$

□

3.c

Plugging in,

$$x_c(t) = x_0 e^{\lambda t} + \int_0^t e^{s\tau} e^{\lambda(t-\tau)} d\tau = x_0 e^{\lambda t} + \int_0^t e^{(s-\lambda)\tau + \lambda t} d\tau \quad (21)$$

$$= x_0 e^{\lambda t} + \frac{1}{s-\lambda} e^{(s-\lambda)\tau + \lambda t} \Big|_0^t \quad (22)$$

$$= x_0 e^{\lambda t} + \left(\frac{1}{s-\lambda} e^{st - \lambda t + \lambda t} \right) - \left(\frac{1}{s-\lambda} e^{\lambda t} \right) \quad (23)$$

$$= x_0 e^{\lambda t} + \frac{1}{s-\lambda} (e^{st} - e^{\lambda t}) \quad (24)$$

3.d


Plugging in,

$$x_c(t) = x_0 e^{\lambda t} + \int_0^t e^{\lambda\tau} e^{\lambda(t-\tau)} d\tau = x_0 e^{\lambda t} + \int_0^t e^{\lambda t} d\tau \quad (25)$$

$$= x_0 e^{\lambda t} + t e^{\lambda t} \quad (26)$$

4 Op-Amp Stability

4.a

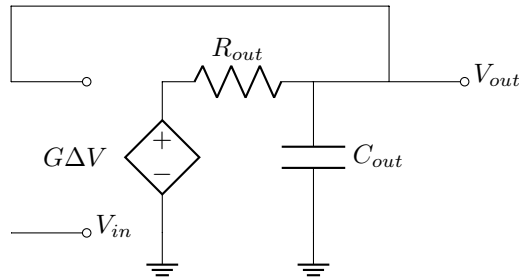

4.b

The KCL equation for V_{out} is

$$C_{out} \frac{d}{dt} V_{out} - \frac{G(V_{in} - V_{out}) - V_{out}}{R_{out}} = 0 \quad (27)$$

$$\frac{d}{dt} V_{out} = \frac{GV_{in} - (G+1)V_{out}}{R_{out}C_{out}} = \frac{G+1}{R_{out}C_{out}} \left(\frac{G}{G+1} V_{in} - V_{out} \right) \quad (28)$$

$$\int \frac{1}{\frac{G}{G+1} V_{in} - V_{out}} dV_{out} = \int \frac{G+1}{R_{out}C_{out}} dt \quad (29)$$

$$-\ln \left| \frac{G}{G+1} V_{in} - V_{out} \right| = \frac{G+1}{R_{out}C_{out}} t + K \quad (30)$$

$$V_{out}(t) = \frac{G}{G+1} V_{in} - V_0 \exp \left(-\frac{G+1}{R_{out}C_{out}} t \right) \quad (31)$$

$$\lim_{t \rightarrow \infty} V_{out}(t) = \frac{G}{G+1} V_{in} \quad (32)$$

4.c

Using similar techniques,

$$C_{out} \frac{d}{dt} V_{out} - \frac{G(V_{out} - V_{in}) - V_{out}}{R_{out}} = 0 \quad (33)$$

$$\frac{d}{dt} V_{out} = \frac{(G-1)V_{out} - GV_{in}}{R_{out}C_{out}} = \frac{G-1}{R_{out}C_{out}} \left(V_{out} - \frac{G}{G-1} V_{in} \right) \quad (34)$$

$$\int \frac{1}{V_{out} - \frac{G}{G-1} V_{in}} dV_{out} = \int \frac{G-1}{R_{out}C_{out}} dt \quad (35)$$

$$\ln \left| V_{out} - \frac{G}{G-1} V_{in} \right| = \frac{G-1}{R_{out}C_{out}} t + K \quad (36)$$

$$V_{out}(t) = \frac{G}{G-1} V_{in} + V_0 \exp \left(\frac{G-1}{R_{out}C_{out}} t \right) \quad (37)$$

$$\lim_{t \rightarrow \infty} V_{out}(t) = \pm \infty \quad (38)$$

Depending on the initial condition, the op-amp will rail either to the positive or negative. In fact, for $V_{in} > 0$, the op-amp will rail negative due to the fact that when we solve for the initial condition, $V_0 = -\frac{G}{G-1} V_{in} < 0$.

4.d

Given the $V_{out}(t)$ from 4.b,

$$\lim_{G \rightarrow \infty} V_{out}(t) = V_{in} - V_0 \exp \left(\lim_{G \rightarrow \infty} \frac{G+1}{R_{out}C_{out}} t \right) = V_{in} \quad (39)$$

6 Homework Process and Study Group

1. I referred to my lecture notes.
2. I did this homework by myself.
3. I worked on this homework in one sitting, and revised it the day after.
4. 4 hours.