

# EECS 16B HW04

Bryan Ngo

2020-02-25

## 1 Phasors


### 1.a

$$Z_R = R = 1.5 \Omega \quad (1)$$

$$Z_C = \frac{1}{j\omega C} = -\frac{j}{\omega} \Omega \quad (2)$$

$$Z_L = j\omega L = j\omega \Omega \quad (3)$$


### 1.b

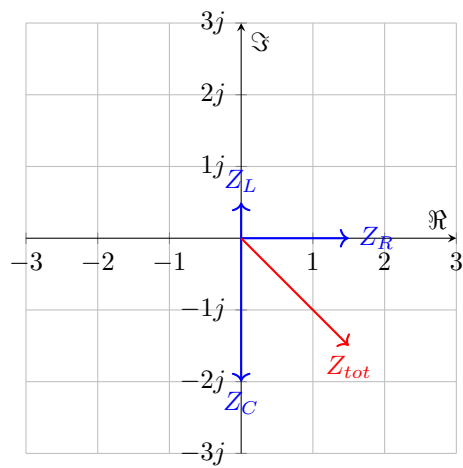

$$|Z_{tot}| = 1.5\sqrt{2} \Omega \quad (4)$$

$$\theta = -\frac{\pi}{4} \text{ rad} \quad (5)$$


1.c

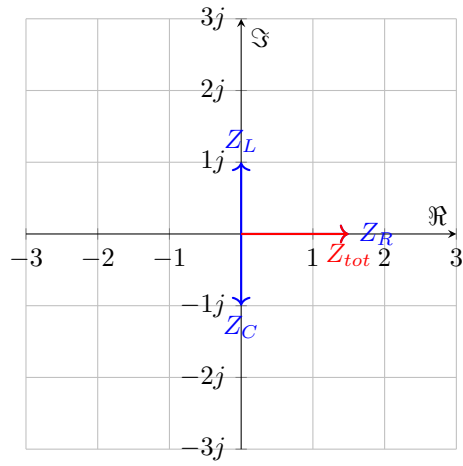

$$|Z_{tot}| = 1.5 \Omega \quad (6)$$

$$\theta = 0 \text{ rad} \quad (7)$$

1.d

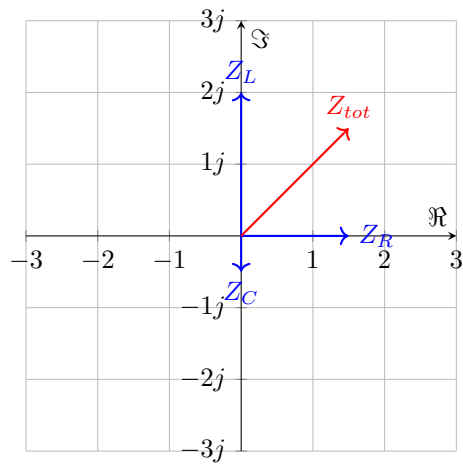


$$|Z_{tot}| = 1.5\sqrt{2} \Omega \quad (8)$$

$$\theta = \frac{\pi}{4} \text{ rad} \quad (9)$$

1.e


$$\omega_n = 1 \text{ rad s}^{-1}$$

## 2 Low-pass Filter

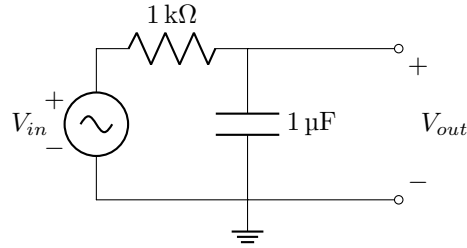

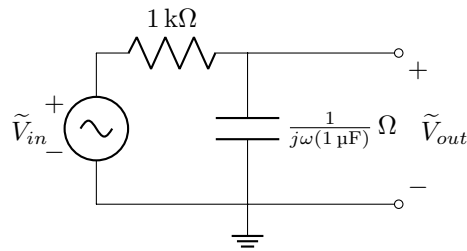**2.a**

Phasorizing, the circuit is now transformed into



**2.b**

$$H(j\omega) = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \underbrace{\frac{\frac{1}{j\omega(1\mu\text{F})}}{1\text{ k}\Omega + \frac{1}{j\omega(1\mu\text{F})}}}_{\text{voltage divider}} = \frac{1}{1 + (1\text{ k}\Omega)j\omega(1\mu\text{F})} = \frac{1}{1 + j\omega(1\text{ ms})} \quad (10)$$

**2.c**

$$H(j \times 10^6 \text{ rad s}^{-1}) = \frac{1}{1 + (j \times 10^6 \text{ rad s}^{-1})(1\text{ ms})} = \frac{1}{1 + j \times 10^3} \approx (0.001 + j) \times 10^{-3} \quad (11)$$

$$\Rightarrow |H(j \times 10^6 \text{ rad s}^{-1})| \approx 10^{-3} \Omega \quad (12)$$

**2.d**

$$H(j \text{ rad s}^{-1}) = \frac{1}{1 + (j \text{ rad s}^{-1})(1\text{ ms})} = \frac{1}{1 + j \times 10^{-3}} \approx (1 + 0.001j) \times 10^{-3} \quad (13)$$

$$\angle H(j \text{ rad s}^{-1}) \approx -10^{-3} \text{ rad} \quad (14)$$

## 2.e

Since the input is a sine wave, our input  $V_{in}(t) = \Re\{e^{j\frac{\pi}{2}}e^{1000jt}\}$ . Then,

$$\tilde{V}_{out}\Big|_{\omega=1000} = \frac{1}{1+j}\tilde{V}_{in} \quad (15)$$

$$V_{out}(t) = \Re\left\{\tilde{V}_{out}e^{1000jt}\right\} \quad (16)$$


$$= \Re\left\{\frac{1}{1+j}\tilde{V}_{in}e^{1000jt}\right\} \quad (17)$$

$$= \Re\left\{\frac{1}{1+j}e^{j\frac{\pi}{2}}e^{1000jt}\right\} \quad (18)$$

$$= \Re\left\{\frac{1}{|1+j|}e^{-j\frac{\pi}{4}}e^{j\frac{\pi}{2}}e^{1000jt}\right\} \quad (19)$$

$$= \frac{1}{\sqrt{2}}\cos\left(1000t + \frac{\pi}{4}\right) \quad (20)$$

## 2.f

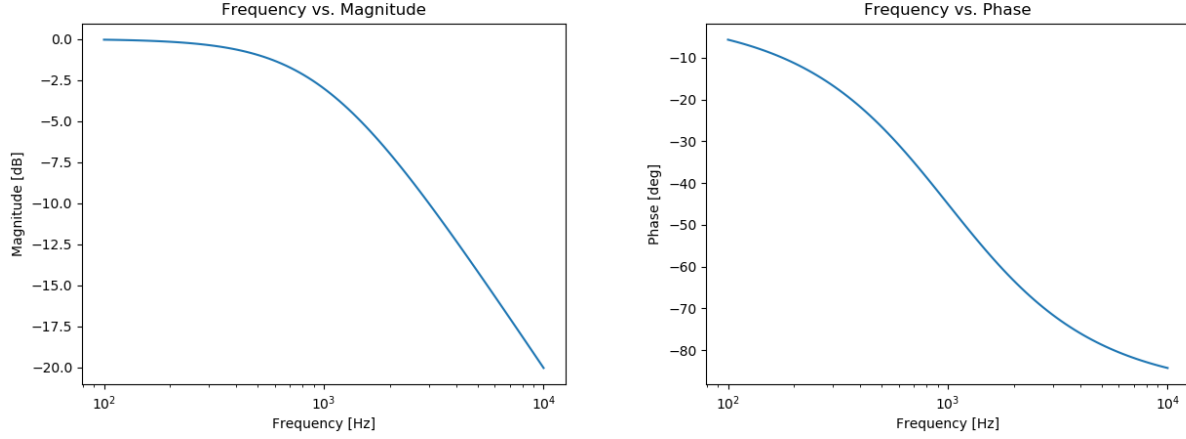

## 3 Color Organ Filter Design


### 3.a

For the low-pass filter, the cutoff frequency is

$$f_{cut} = \frac{1}{2\pi RC} \Rightarrow R = \frac{1}{2\pi f_{cut}C} = 66\ \Omega \quad (21)$$

For the high-pass filter,
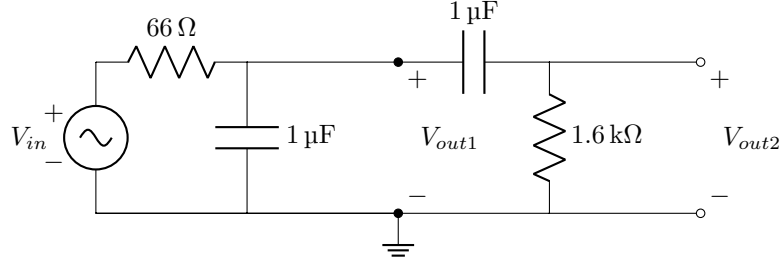
$$f_{cut} = \frac{1}{2\pi RC} \Rightarrow R = \frac{1}{2\pi f_{cut}C} = 1.6\text{ k}\Omega \quad (22)$$



### 3.b


Since there is no buffer, we cannot simply take the product. Using equivalent impedance, the voltage  $V_{out1}$  is

$$V_{out1} = \frac{(R_H + \frac{1}{j\omega C_H}) \parallel \frac{1}{j\omega C_L}}{(R_H + \frac{1}{j\omega C_H}) \parallel \frac{1}{j\omega C_L} + R_L} V_{in} \quad (23)$$

Meaning that

$$V_{out2} = \frac{j\omega R_H C_H}{1 + j\omega R_H C_H} \frac{(R_H + \frac{1}{j\omega C_H}) \parallel \frac{1}{j\omega C_L}}{(R_H + \frac{1}{j\omega C_H}) \parallel \frac{1}{j\omega C_L} + R_L} V_{in} \quad (24)$$

### 3.c

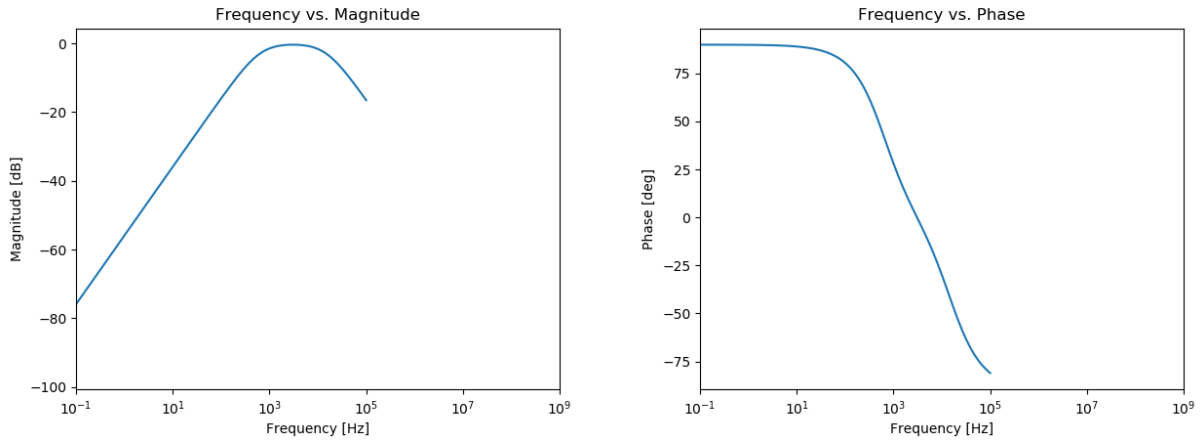

The numerator becomes zero when  $\omega = 0$ . The denominator becomes 0 when  $\omega = \frac{j}{R_L C_L}, \frac{j}{R_H C_H}$ . The maximum magnitude is 0, which makes sense because we cannot amplify the signal with passive elements.

### 3.d

First, we find  $K_{mic}$ , which is

$$\frac{1}{2} V_{pp} = K_{mic} \frac{j\omega \left(1 + \frac{j\omega}{\omega_{z1}}\right)}{\left(1 + \frac{j\omega}{\omega_{p1}}\right) \left(1 + \frac{j\omega}{\omega_{p2}}\right) \left(1 + \frac{j\omega}{\omega_{p3}}\right)} \quad (25)$$

$$\Rightarrow K_{mic} = \frac{\left(1 + \frac{j\omega}{\omega_{p1}}\right) \left(1 + \frac{j\omega}{\omega_{p2}}\right) \left(1 + \frac{j\omega}{\omega_{p3}}\right)}{2j\omega \left(1 + \frac{j\omega}{\omega_{z1}}\right)} V_{pp} \approx (8.6 - 0.5j) \text{ mV} \quad (26)$$

Then, we plug  $V_{mic}$  as the input voltage into the filters,

$$V_{LP} = \frac{2}{1 + \frac{j\omega}{200\pi}} V_{mic} \quad (27)$$

$$V_{BP} = \frac{4.54 \times 10^{-4} j\omega}{\left(1 + \frac{j\omega}{400\pi}\right) \left(1 + \frac{j\omega}{4000\pi}\right)} V_{mic} \quad (28)$$

$$V_{HP} = \frac{\frac{j\omega}{8000\pi}}{1 + \frac{j\omega}{8000\pi}} V_{mic} \quad (29)$$

### 3.e

With  $V_{pp} = 5 \text{ V}$ , we want our amplitude of the phasor to be  $2.5 \text{ V}$  outside the amplifier. Thus,  $G = \frac{2.5}{|V_{out}|}$ . At  $50 \text{ Hz}$ ,

$$|V_{LP}(2\pi \cdot 50)| \approx 1.76 \text{ V} \Rightarrow G = 1.42 \quad (30)$$

$$|V_{BP}(2\pi \cdot 50)| \approx 0.136 \text{ V} \Rightarrow G = 18.4 \quad (31)$$

$$|V_{HP}(2\pi \cdot 50)| \approx 12.3 \text{ mV} \Rightarrow G = 203 \quad (32)$$

At  $1000 \text{ Hz}$ ,

$$|V_{LP}(2\pi \cdot 1000)| \approx 0.109 \text{ V} \Rightarrow G = 22.9 \quad (33)$$

$$|V_{BP}(2\pi \cdot 1000)| \approx 0.275 \text{ V} \Rightarrow G = 9.09 \quad (34)$$

$$|V_{HP}(2\pi \cdot 1000)| \approx 0.133 \text{ V} \Rightarrow G = 18.7 \quad (35)$$

At  $8000 \text{ Hz}$ ,

$$|V_{LP}(2\pi \cdot 8000)| \approx 10.6 \text{ mV} \Rightarrow G = 235 \quad (36)$$

$$|V_{BP}(2\pi \cdot 8000)| \approx 58.8 \text{ mV} \Rightarrow G = 42.5 \quad (37)$$

$$|V_{HP}(2\pi \cdot 8000)| \approx 0.380 \text{ V} \Rightarrow G = 6.57 \quad (38)$$

## 4 Mystery Microphone

### 4.a

The microphone is most sensitive at frequencies  $3 \times 10^2 \text{ Hz}$ — $5 \times 10^3 \text{ Hz}$ . The microphone is least sensitive mostly everywhere else, particularly  $10 \text{ Hz}$ — $70 \text{ Hz}$ .

### 4.b

You would have the best time hearing the mid-range frequencies, since the mic is most responsive to those frequencies, and have a harder time hearing the lower-end and higher-end frequencies.

### 4.c

I would apply an amplification block for frequencies  $10 \text{ Hz}$ — $70 \text{ Hz}$  with an amplifier gain of  $12.5$ . I would also apply an amplification block for frequencies above  $10^4 \text{ Hz}$  with an amplifier gain of  $1.67$ .

## 6 Homework Process and Study Group

1. I used lecture note 2020-02-13 and Note 5.
2. I worked on this homework by myself.
3. I worked on this homework in one sitting.
4. 4 hours.