

EECS 16B HW03

Bryan Ngo

2020-02-18

1 Complex Numbers

1.a Length of z

$$|z| = \sqrt{x^2 + y^2} \quad (1)$$

1.b Polar Representation


$$\Re(z) = x = r \cos(\theta) \quad (2)$$

$$\Im(z) = y = r \sin(\theta) \quad (3)$$

1.c Euler's Formula

$$z = x + jy = r \cos(\theta) + jr \sin(\theta) = r(\cos(\theta) + j \sin(\theta)) = re^{j\theta} \quad (4)$$

1.d Unit Complex Circle

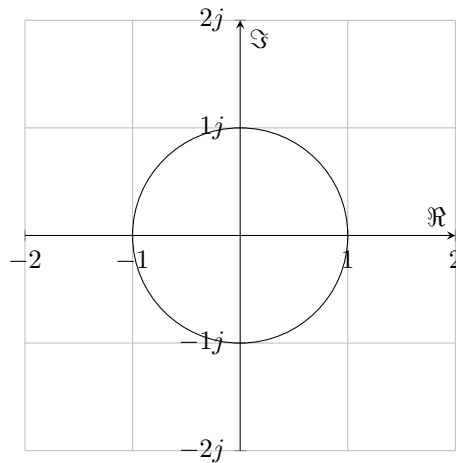

z intersects the real axis at $z = \pm 1$. z intersects the imaginary axis at $z = \pm j$.

1.e

Proof.

$$z = re^{j\theta} \quad (5)$$

$$re^{-j\theta} = r \cos(-\theta) + jr \sin(-\theta) \quad (6)$$

$$= r \cos(\theta) - jr \sin(\theta) \quad (7)$$

$$= x - jy = \bar{z} \quad (8)$$

□

1.f

Proof.


$$z\bar{z} = (x + jy)(x - jy) \quad \text{definition of conjugate multiplication} \quad (9)$$

$$= x^2 - (jy)^2 \quad \text{difference of squares} \quad (10)$$

$$= x^2 + y^2 = r^2 \quad \text{definition of } j \quad (11)$$

□

2 RLC Responses: Initial Part

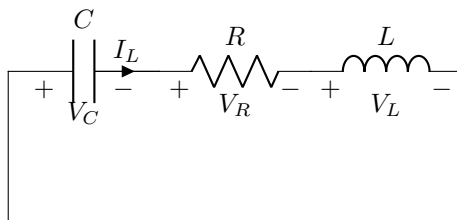

2.a

Using KVL,

$$V_C + V_R + L \frac{d}{dt} I_L = 0 \quad (12)$$

$$C \frac{d}{dt} V_C = I_L \quad (13)$$

Using simple algebra, we can rearrange to

$$\frac{d}{dt} I_L = -\frac{1}{L} (RI_L + V_C) \quad (14)$$

$$\frac{d}{dt} V_C = \frac{1}{C} I_L \quad (15)$$

2.b

$$\frac{d}{dt} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} = \begin{bmatrix} -\frac{R}{L} & -\frac{1}{L} \\ \frac{1}{C} & 0 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} \quad (16)$$

2.c

$$\begin{vmatrix} -\frac{R}{L} - \lambda & -\frac{1}{L} \\ \frac{1}{C} & -\lambda \end{vmatrix} = \lambda^2 + \frac{R}{L}\lambda + \frac{1}{LC} = 0 \quad (17)$$

$$\lambda = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \quad (18)$$

2.d

$$\lambda \in \mathbb{R} \iff \frac{R^2}{4L^2} - \frac{1}{LC} \geq 0 \quad (19)$$

2.e

$$\lambda \in \{jk | k \in \mathbb{R}, j^2 = -1\} \iff R = 0 \wedge \frac{1}{LC} \geq 0 \quad (20)$$

2.f

Finding the eigenvectors,

$$\begin{bmatrix} -\frac{R}{2L} - \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} & -\frac{1}{L} \\ \frac{1}{C} & \frac{R}{2L} - \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \end{bmatrix} \begin{bmatrix} 1 \\ y \end{bmatrix} = \left(-\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \right) \begin{bmatrix} 1 \\ y \end{bmatrix} \quad (21)$$

$$\Rightarrow y_1 = -2L\sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \quad (22)$$

$$\mathbf{v}_1 = \begin{bmatrix} 1 \\ -2L\sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \end{bmatrix} \quad (23)$$


$$\Rightarrow y_2 = 2L\sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \quad (24)$$

$$\mathbf{v}_2 = \begin{bmatrix} 1 \\ 2L\sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \end{bmatrix} \quad (25)$$

2.g

$$\frac{d}{dt}\mathbf{z}(t) = \begin{bmatrix} \lambda_1 & 0 \\ 0 & \lambda_2 \end{bmatrix} \mathbf{z}(t) \quad (26)$$

3 RLC Responses: Overdamped Case

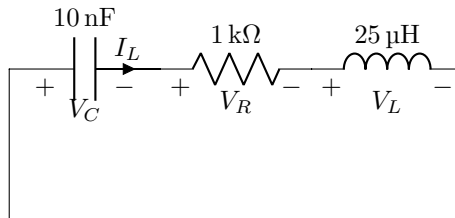

3.a

$$\mathbf{V} \approx \begin{bmatrix} 1 & 1 \\ -995 & 995 \end{bmatrix} \quad (27)$$

$$\mathbf{z}(0) = \mathbf{V}^{-1} \begin{bmatrix} 0 \text{ A} \\ 1 \text{ V} \end{bmatrix} \approx \begin{bmatrix} -502 \times 10^{-6} \\ 502 \times 10^{-6} \end{bmatrix} \quad (28)$$

3.b



$$\lambda_1 \approx -100 \text{ ks}^{-1} \quad (29)$$

$$\lambda_2 \approx -40 \text{ Ms}^{-1} \quad (30)$$

$$\mathbf{z}(t) = \begin{bmatrix} e^{\lambda_1 t} \\ e^{\lambda_2 t} \end{bmatrix} \quad (31)$$


$$\mathbf{x}(t) = \mathbf{V}\mathbf{z}(t) \approx \begin{bmatrix} 1 & 1 \\ -995 & 995 \end{bmatrix} \begin{bmatrix} e^{\lambda_1 t} \\ e^{\lambda_2 t} \end{bmatrix} = \begin{bmatrix} e^{\lambda_1 t} + e^{\lambda_2 t} \\ -995e^{\lambda_1 t} + 995e^{\lambda_2 t} \end{bmatrix} \quad (32)$$

3.c

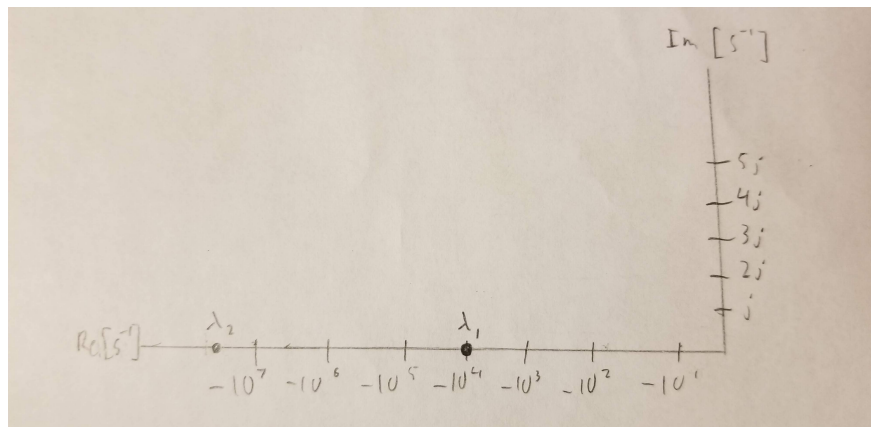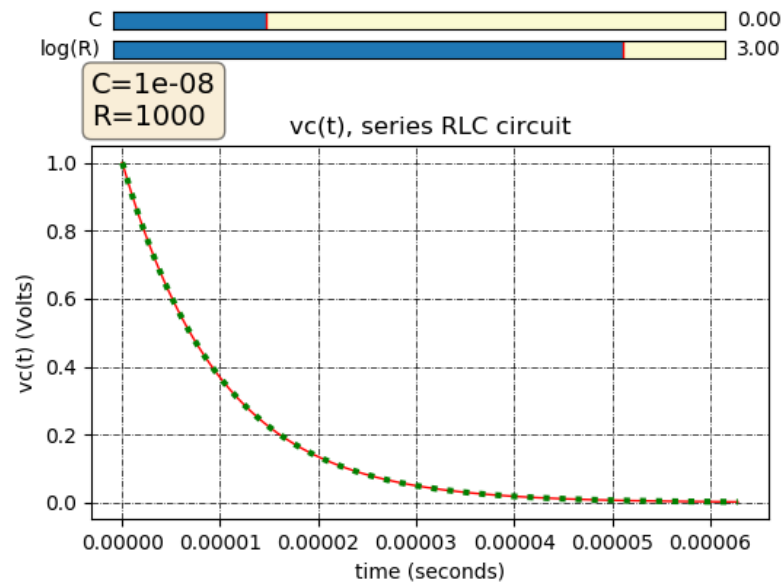

The graph seems to be a plain exponential curve, due to the heavy damping of the resistor.

4 RLC Responses: Undamped Case

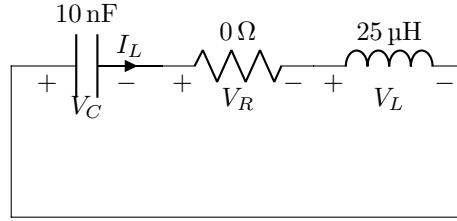

4.a

$$\mathbf{V} \approx \begin{bmatrix} 1 & 1 \\ -100j & 100j \end{bmatrix} \quad (33)$$

$$\mathbf{z}(0) = \mathbf{V}^{-1} \begin{bmatrix} 0 \text{ A} \\ 1 \text{ V} \end{bmatrix} \approx \frac{1}{200} \begin{bmatrix} -1 \\ 1 \end{bmatrix} \quad (34)$$

4.b


$$\lambda_1 = 2j \text{ Ms}^{-1} \quad (35)$$


$$\lambda_2 = -2j \text{ Ms}^{-1} \quad (36)$$

$$\mathbf{z}(t) = \begin{bmatrix} e^{\lambda_1 t} \\ e^{\lambda_2 t} \end{bmatrix} \quad (37)$$

$$\mathbf{x}(t) = \mathbf{V}\mathbf{z}(t) = \begin{bmatrix} 1 & 1 \\ -100j & 100j \end{bmatrix} \begin{bmatrix} e^{\lambda_1 t} \\ e^{\lambda_2 t} \end{bmatrix} = \begin{bmatrix} e^{\lambda_1 t} + e^{\lambda_2 t} \\ -100je^{\lambda_1 t} + 100je^{\lambda_2 t} \end{bmatrix} \quad (38)$$


4.c

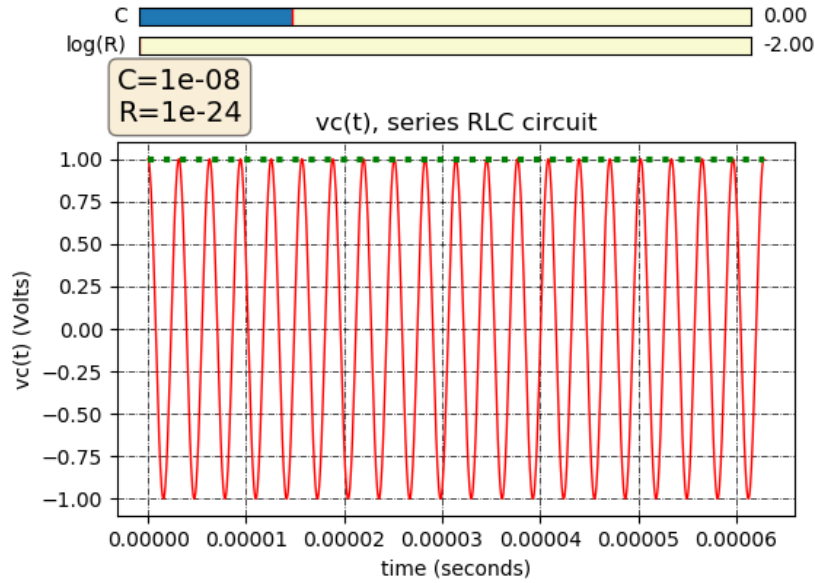

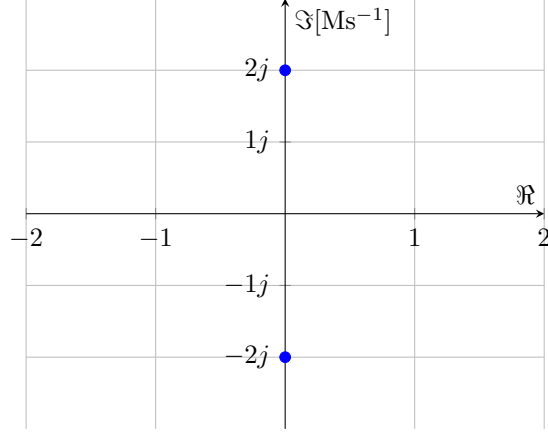

The case here shows that the circuit is *not* transient.

5 RLC Responses: Underdamped Case

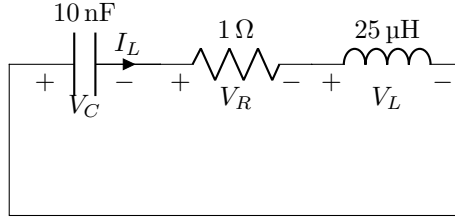

5.a

$$\mathbf{V} \approx \begin{bmatrix} 1 & 1 \\ -100j & 100j \end{bmatrix} \quad (39)$$

$$\mathbf{z}(0) = \mathbf{V}^{-1} \begin{bmatrix} 0 \text{ A} \\ 1 \text{ V} \end{bmatrix} \approx \frac{1}{200} \begin{bmatrix} -1 \\ 1 \end{bmatrix} \quad (40)$$

5.b



$$\lambda_1 = (-20 + 2000j) \text{ ks}^{-1} \quad (41)$$

$$\lambda_2 = (-20 - 2000j) \text{ ks}^{-1} \quad (42)$$

$$\mathbf{z}(t) = \begin{bmatrix} e^{\lambda_1 t} \\ e^{\lambda_2 t} \end{bmatrix} \quad (43)$$

$$\mathbf{x}(t) = \mathbf{V}\mathbf{z}(t) = \begin{bmatrix} 1 & 1 \\ -100j & 100j \end{bmatrix} \begin{bmatrix} e^{\lambda_1 t} \\ e^{\lambda_2 t} \end{bmatrix} = \begin{bmatrix} e^{\lambda_1 t} + e^{\lambda_2 t} \\ -100je^{\lambda_1 t} + 100je^{\lambda_2 t} \end{bmatrix} \quad (44)$$

5.c

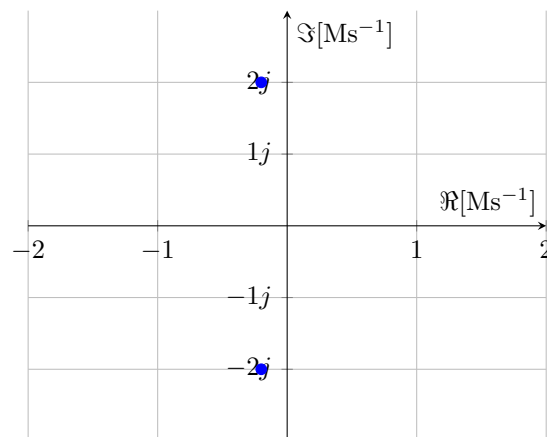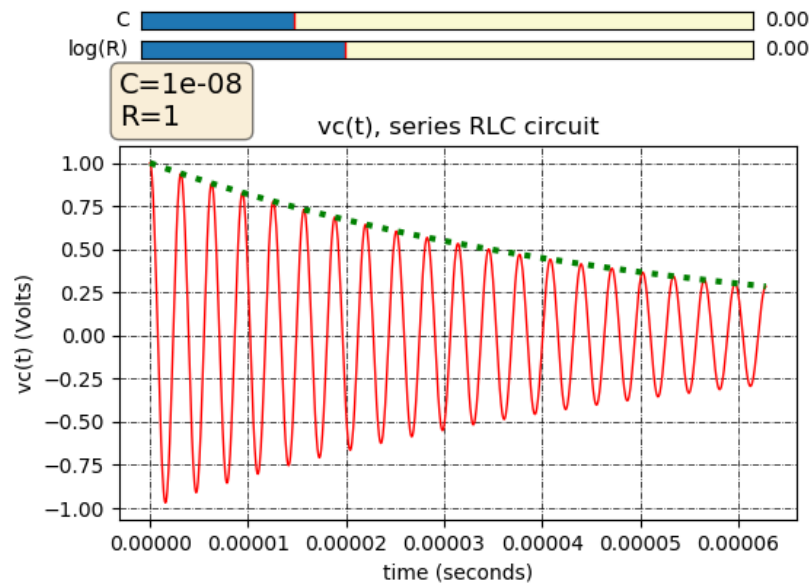

The graph appears to exhibit transient behavior, due to the asymptotic decline.

5.d

Even though $\lambda_1, \lambda_2 \in \mathbb{C}$, it can be shown that the differential equation is nothing more than a linear combination of sine and cosine waves multiplied by an exponential function, due to the fact that

$$\sin(t) = \frac{e^{jt} - e^{-jt}}{2j} \quad (45)$$

$$\cos(t) = \frac{e^{jt} + e^{-jt}}{2} \quad (46)$$

6 RLC Responses: Critically Damped

6.a

There will only be one eigenvalue of A when $\frac{R^2}{4L^2} = \frac{1}{LC} \Rightarrow R = 2\sqrt{\frac{L}{C}}$.

6.b

$$\begin{vmatrix} -\frac{2}{L}\sqrt{\frac{L}{C}} - \lambda & -\frac{1}{L} \\ \frac{1}{C} & -\lambda \end{vmatrix} = \lambda^2 + \frac{2}{L}\sqrt{\frac{L}{C}}\lambda + \frac{1}{LC} = 0 \quad (47)$$


$$\lambda = -2\frac{1}{\sqrt{LC}} \quad (48)$$

$$\begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & \frac{2}{\sqrt{LC}} \end{bmatrix} \begin{bmatrix} 1 \\ y \end{bmatrix} = -\frac{2}{\sqrt{LC}} \begin{bmatrix} 1 \\ y \end{bmatrix} \quad (49)$$

$$y = \frac{2L}{\sqrt{LC}}, -\frac{\sqrt{LC}}{4C} \quad (50)$$

Thus, we are able to find 2 eigenvectors for the eigenspace.

6.c

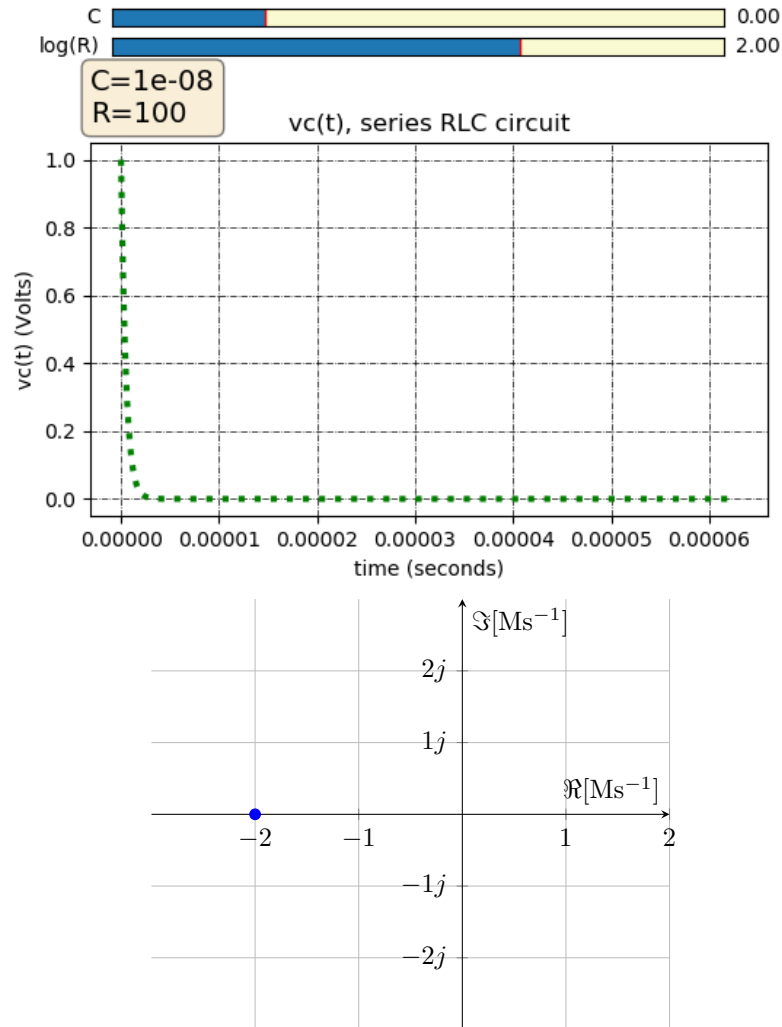

The graph seems to decay faster than at any other eigenvalue. If R is shifted up, then it becomes overdamped and the curve shallows. If R is shifted down, then it becomes underdamped and begins to oscillate.

8 Homework Process and Study Group

1. I referred to Note 3, Discussion 3B, and my lecture notes.
2. I worked on this homework by myself.
3. I did this homework in one sitting.
4. Around 4.5 hours.