

EECS 16A HW10

Bryan Ngo

2019-11-06

1 Op-Amp in Negative Feedback

1.a

In an ideal op-amp, $u_+ = u_-$, so $u_+ - u_- = 0$.

1.b

v_x can be treated as the voltage divided from v_{out} across R_1 , or

$$v_x = v_{out} \frac{R_1}{R_1 + R_2} \quad (1)$$

1.c

Performing KCL at the node between R_1, R_2 , $I_{R_2} - I_{R_1} - I_{u_-} = 0$. Since the current into the terminals of an ideal op-amp are always zero, $I_{R_2} = I_{R_1}$. Then, by the fact that $v_s = v_x$

$$I_{R_1} = I_{R_2} = \frac{v_x}{R_1} = \frac{v_s}{R_1} \quad (2)$$

1.d

Given the equation from 1.b,

$$v_x = v_{out} \frac{R_1}{R_1 + R_2} \quad (3)$$

$$\Rightarrow v_{out} = v_x \frac{R_1 + R_2}{R_1} = v_x \left(1 + \frac{R_2}{R_1} \right) \quad (4)$$

$$= v_s \left(1 + \frac{R_2}{R_1} \right) \quad (5)$$

1.e

The current $i_L = \frac{v_{out}}{R}$. By KCL, $i_{VDD} + i_{u+} + i_{u-} - i_{VSS} - i_L = 0$,

$$\begin{cases} i_{VDD} - i_{VSS} = \frac{v_{out}}{R} & v_{out} > 0 \\ i_{VSS} - i_{VDD} = \frac{v_{out}}{R} & v_{out} < 0 \end{cases} \quad (6)$$

1.f

Given the fundamental op-amp equation

$$v_{out} = A(v_s - v_x) \quad (7)$$

$$= A \left(v_s - v_{out} \frac{R_1}{R_1 + R_2} \right) \quad (8)$$

$$v_{out} \left(1 + A \frac{R_1}{R_1 + R_2} \right) = Av_s \quad (9)$$

$$= \frac{Av_s}{1 + A \frac{R_1}{R_1 + R_2}} \cdot \frac{R_1 + R_2}{R_1 + R_2} \quad (10)$$

$$= v_s \frac{A(R_1 + R_2)}{R_2 + R_1(A + 1)} \quad (11)$$

Plugging into the equation for v_x from 1.b,

$$v_x = v_s \frac{A(R_1 + R_2)}{R_2 + R_1(A + 1)} \frac{R_1}{R_1 + R_2} = v_s \frac{AR_1}{R_2 + R_1(A + 1)} \quad (12)$$

This means $v_x < v_s$ for any finite gain, independent of R .

1.g

$$\lim_{A \rightarrow \infty} v_{out} = \lim_{A \rightarrow \infty} v_s \frac{A(R_1 + R_2)}{R_2 + R_1(A + 1)} = v_s \frac{R_1 + R_2}{R_1} = v_s \left(1 + \frac{R_2}{R_1} \right) \quad (13)$$

$$\lim_{A \rightarrow \infty} v_x = \lim_{A \rightarrow \infty} v_s \frac{AR_1}{R_2 + R_1(A + 1)} = v_s \frac{R_1}{R_1} = v_s \quad (14)$$

1.h

Solving for $G_{min} = 1.98$, or the smallest gain,

$$G_{min} = \frac{v_{out}}{v_s} = \frac{A(R_1 + R_2)}{R_2 + R_1(A + 1)} = 1.98 \quad (15)$$


$$A(R_1 + R_2) = 1.98(R_2 + AR_1 + R_1) \quad (16)$$

$$A(R_1 + R_2) - 1.98AR_1 = 1.98(R_1 + R_2) \quad (17)$$

$$A = \frac{1.98(R_1 + R_2)}{0.02R_1 + R_2} \quad (18)$$

2 Capacitive Touchscreen

2.a

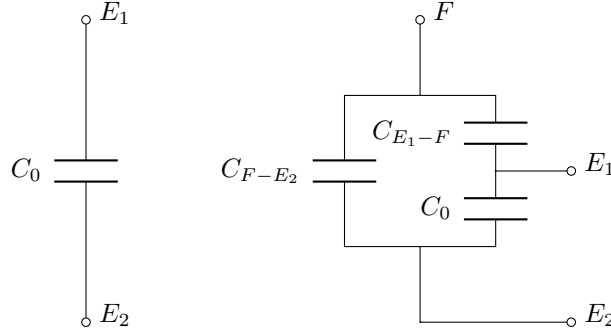

2.b

$$C_0 = \epsilon \frac{w_1 \cdot d_2}{t_1} = 4.43 \times 10^{-14} \text{ F} \quad (19)$$

$$C_{F-E_2} = \epsilon \frac{(w_2 - w_1) \cdot d_2}{t_2} = 2.215 \times 10^{-14} \text{ F} \quad (20)$$

$$C_{E_1-F} = \epsilon \frac{w_1 \cdot d_1}{t_2 - t_1} = 4.43 \times 10^{-13} \text{ F} \quad (21)$$

2.c

Trivially, the capacitance between E_1, E_2 with no finger is C_0 . We can calculate the equivalent capacitance between E_1, E_2 when a finger is present as

$$C_0 + (C_{F-E_2} \parallel C_{E_1-F}) \quad (22)$$

Since $C_{F-E_2}, C_{E_1-F} > 0$, the equivalent capacitance when a finger is present *must* be greater than C_0 , with a difference of $C_{F-E_2} \parallel C_{E_1-F} \approx 2.110 \times 10^{-14} \text{ F}$.

3 Homework Process and Study Group

I did this homework by myself.